

Finite State Machines

Computer Architecture



CS3501 - 2025I

PROF.: JGONZALEZ@UTEC.EDU.PE

SRC: HARRIS, HARRIS - DIGITAL DESIGN AND COMPUTER ARCHITECTURE

Executive Summary

2

- **Motivation:** Combinational circuits with sequential circuits allow to implement a complex design
- **Problem:** We need a procedure to transform our design idea to a circuit
- **Overview:**
 - **State definitions.**
 - Finite State Machine (FSM) design.
 - FSM examples.
- **Conclusion:** A complex idea can be implemented as a digital design using sequential and combinational building blocks

Outline

3

Introduction

Definitions

Finite State Machines


Conclusion

Recall: D Flip-Flop

4

- **Inputs:** WE, D
- **Function**
 - Samples D on rising edge of WE
 - When WE rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of WE
- **Activated on the WE edge** (edge-triggered).

D Flip-Flop Symbols

 


D Flip-Flop operation is associated with a **CLK (clock)** instead of a **WE**.


Recall: D Flip-Flop Internal Circuit

5

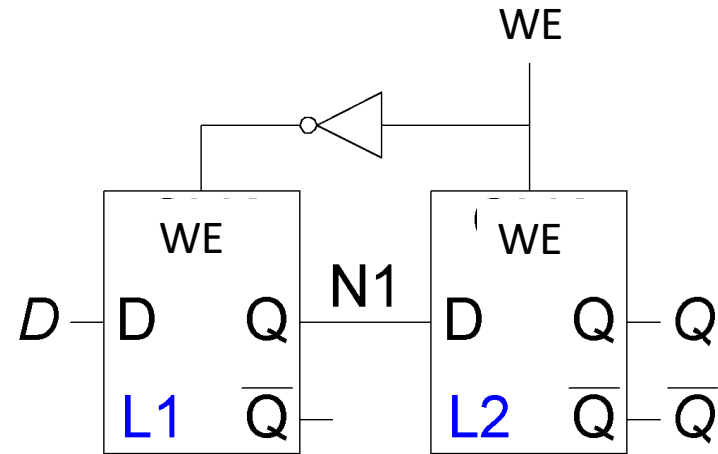- **Two back-to-back latches** (L1 and L2) controlled by **complementary WE**
- When **WE = 0**
 - L1 is transparent
 - L2 is opaque
 - D passes through to N1
- When **WE = 1**
 - L2 is transparent
 - L1 is opaque
 - N1 passes through to Q
- Thus, on the edge of the WE (when **WE rises from 0 → 1**)
 - D passes through to Q



Recall: Gated D Latch vs D Flip-Flop

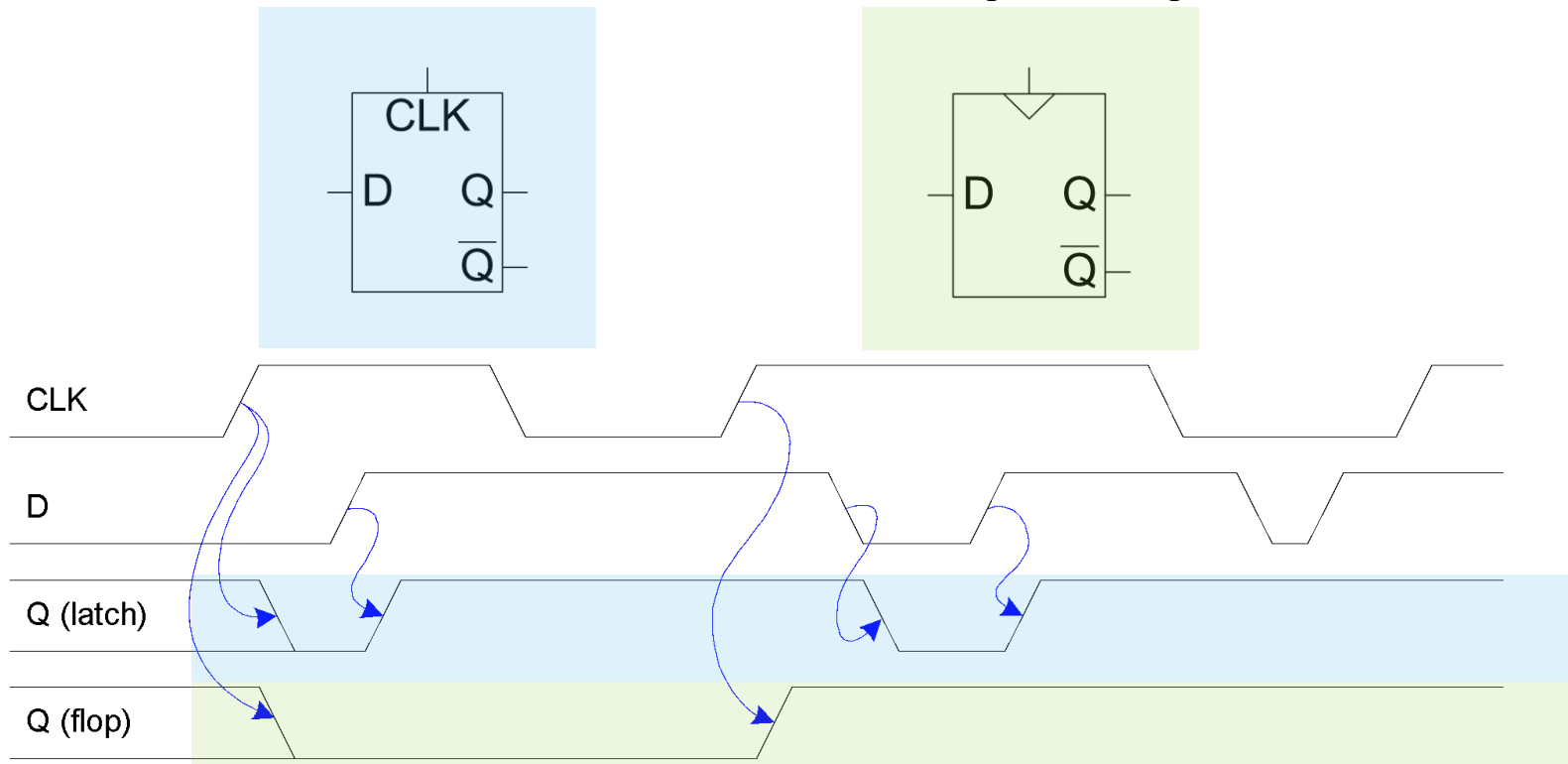

At the lab we use a clock (clk) to change the Q value using D input

Outline

7

Introduction

Definitions

Finite State Machines

Conclusion


State Definitions

8

- **State:**

- **In a system**, it is a **snapshot** of all the important elements (at the time of taking the snapshot).
- **In a circuit**, **all the information about a circuit** necessary to define its future behavior.
 - **State elements:** “store the state” or store one bit (e.g.: latches, flip-flops).

- **Diagram example:** a semaphore

 


State Definitions

9

- **State:**


- **In a system**, it is a **snapshot** of all the important elements (at the time of taking the snapshot).
- **In a circuit**, **all the information about a circuit** necessary to define its future behavior.
 - **State elements:** “store the state” or store one bit (e.g.: latches, flip-flops).

- **Diagram example:** a semaphore

 

State Transition

10

 

- **Clock** is a general mechanism that **triggers transition from one state to another** in a sequential circuit
 - Clock **synchronizes state changes** across many sequential circuit elements
 - Combinational logic evaluates for the length of the clock cycle
- CLK:
- **At the start of a clock cycle** (), system state changes
 - **During a clock cycle, the state stays constant**
 - In the semaphore example, **we are assuming the traffic light stays in each state an equal amount of time**

Outline

11

Introduction

Definitions

Finite State Machines

Conclusion

Finite State Machine (FSM)

12

- A **discrete-time model of a stateful system**
- Each state represents a **snapshot** of the system at a given time
- **Can model** a semaphore, washing machine, a computer processor, etc.
- An **FSM state diagram can visually represent**:
 1. All possible states
 2. Transition conditions
- It is **defined as finite because** it has:
 1. A **finite** number of states (snapshot)
 2. A **finite** number of external inputs
 3. A **finite** number of external outputs
 4. An explicit specification of all state transitions
 5. An explicit specification of what determines each external output value


FSM Elements

13

- **Sequential Circuits**

- **State register**

 
- Stores current state
 - Loads next state at clock edge



- **Combinational Circuits**


- **Next state logic:**

- Computes the next state

 

- **Output logic:**

- Computes the outputs

 

State Register Implementation

14


- How can we implement a **state register**? Two properties:

1. We need to store data at the **beginning** of every clock cycle

*Clock transition determines
when input is acquired*



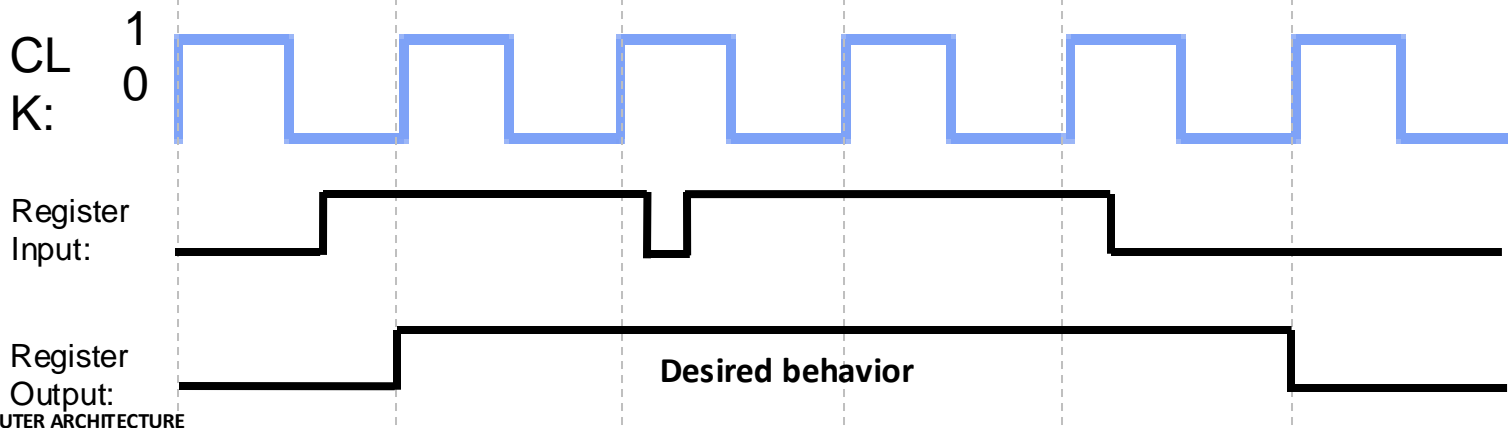
2. The data must be **available** during the entire clock cycle




Problem: State Register with Latches

15

Recall the
Gated D Latch

 

 
- If we wire a clock to WE of a latch
 - **Whenever the clock is high, the latch propagates D to Q**
 - **The latch is transparent**



Solution: State Register with D Flip-Flop

16

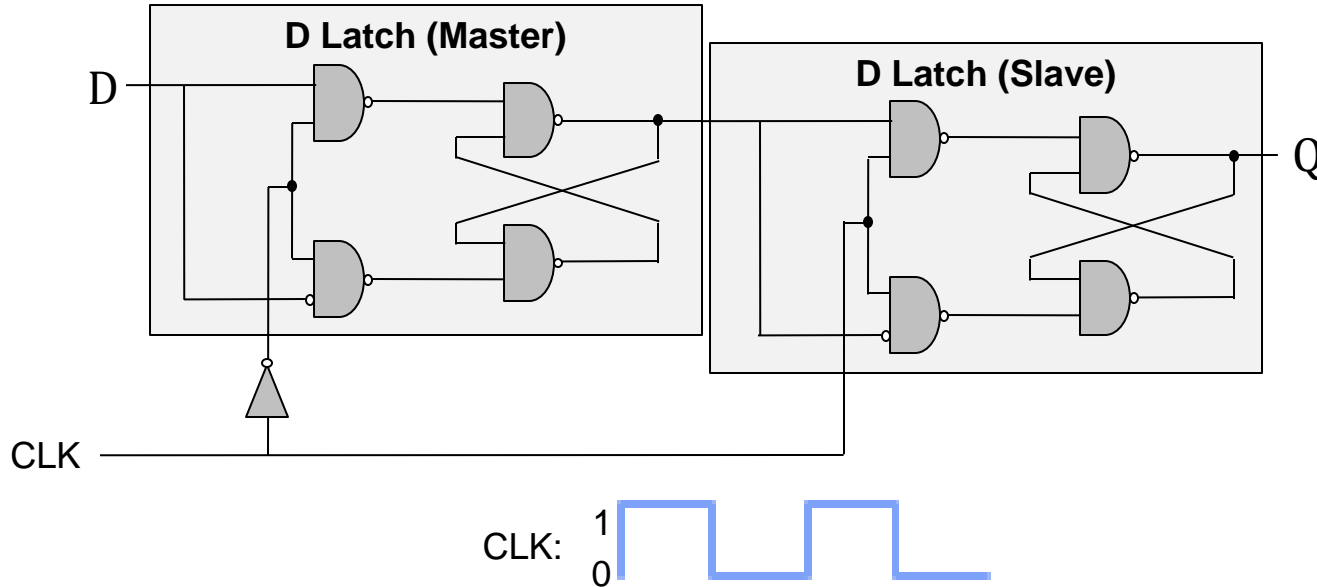- 1) state change on clock edge, 2) data available for full cycle




- **When the clock is low**, master propagates **D** to the input of slave (Q unchanged)
- **Only when the clock is high**, slave latches **D** (Q stores D)
 - At the rising edge of clock (clock going from 0→1), Q gets assigned D

Recall: D Flip-Flop

17

- **Inputs:** WE, D
- **Function**
 - Samples D on rising edge of WE
 - When WE rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of WE
- **Activated on the WE edge** (edge-triggered).

D Flip-Flop Symbols

 


D Flip-Flop operation is associated with a **CLK (clock)** instead of a WE.

We will explain the clock in later lectures.

Recall: Gated D Latch vs D Flip-Flop



18

 

At the lab we use a clock (clk) to change the Q value using D input

Recall: 4-bit Register with D Flip Flop

19

  


Types of FSM

20


- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 1. **Moore FSM: outputs depend only on current state**

Moore FSM

 

1. **Mealy FSM: outputs depend on current state *and* inputs**

Mealy FSM

 

FSM example

21

- Design a modulo 8 Gray code counter with an UP/DOWN counter. Define an UP input. If $UP = 1$, the counter advances to the next number. If $UP = 0$, the counter retreats to the previous number.
- Add an output Y, where $Y = 1$ every time the Gray count has only one zero.


FSM Black Box

22

- **Inputs:** ?
- **Outputs:** ?

1. Design the state diagram

23

 

2. Write down the next state logic

24

current state $s_{2:0}$	input up	next state $s'_{2:0}$
000	1	001
001	1	011
011	1	010
010	1	110
110	1	111
111	1	101
101	1	100
100	1	000
000	0	100
001	0	000
011	0	001
010	0	011
110	0	010
111	0	110
101	0	111
100	0	101

$$S_2 = UPS_1\bar{S}_0 + \overline{UP}\bar{S}_1\bar{S}_0 + S_2S_0$$

$$S_1 = S_1\bar{S}_0 + UPS_2S_0 + \overline{UP}S_2S_1$$


$$S_0 = UP \oplus S_2 \oplus S_1$$

3. Write down the output logic

25

4. Draw the schematic


26

 

Another FSM Example

27

 
- Traffic light controller
 - **Inputs:**
 - Traffic sensors: T_A , T_B
(TRUE when there's traffic)
 - **Outputs:**
 - Lights: L_A , L_B
 - **States:** transitions each 5 seconds



FSM Black Box

28


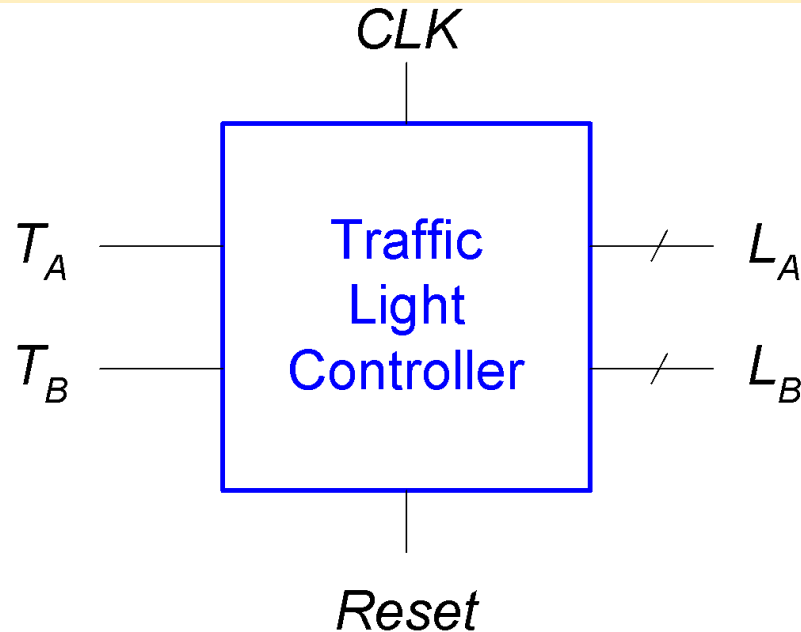
- **Inputs:** CLK , $Reset$, T_A , T_B
- **Outputs:** L_A , L_B



FSM State Transition Diagram

29

 
 
- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Diagram

30

 
 
- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Diagram

31

 
 
- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Diagram


32

  - **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Table


33

 

Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

FSM State Transition Table


34

 

Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

FSM Encoded State Transition Table

35

 


Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

36

 

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (S_1 \cdot S_0) + (S_1 \cdot S_0 \cdot T_B) + (S_1 \cdot S_0 \cdot T_B)$$

$$S'_0 = (S_1 \cdot S_0 \cdot T_A) + (S_1 \cdot S_0 \cdot T_B)$$

FSM Encoded State Transition Table

37

 

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} \overline{T_B}$$

FSM Output Table

38

 


Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0				
0	1				
1	0				
1	1				

Output	Encoding
green	00
yellow	01
red	10

FSM Output Table

39

 

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1


Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$

$$L_{A0} = S_1 \cdot S_0$$

FSM Output Table

40

 

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$


$$L_{A0} = S_1 \cdot S_0$$

$$L_{B1} = S_1$$

$$L_{B0} = S_1 \cdot S_0$$


FSM Schematic: State Register

41

 

FSM Schematic: Next State Logic


42

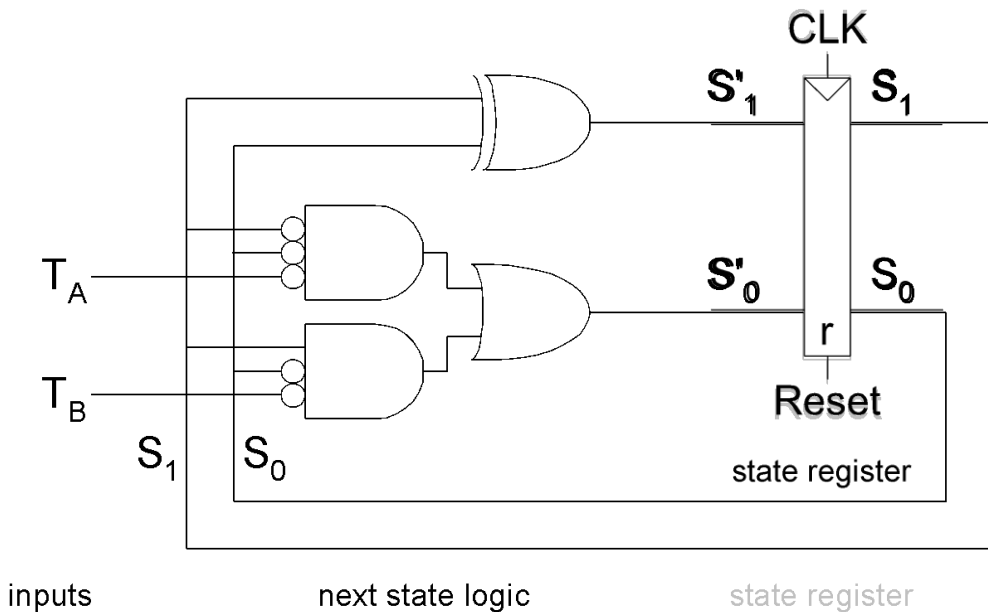

$$S'_1 = S_1 \text{ xor } S_0$$

$$S'_0 = (S_1 \cdot S_0 \cdot T_A) + (S_1 \cdot S_0 \cdot T_B)$$

FSM Schematic: Output Logic

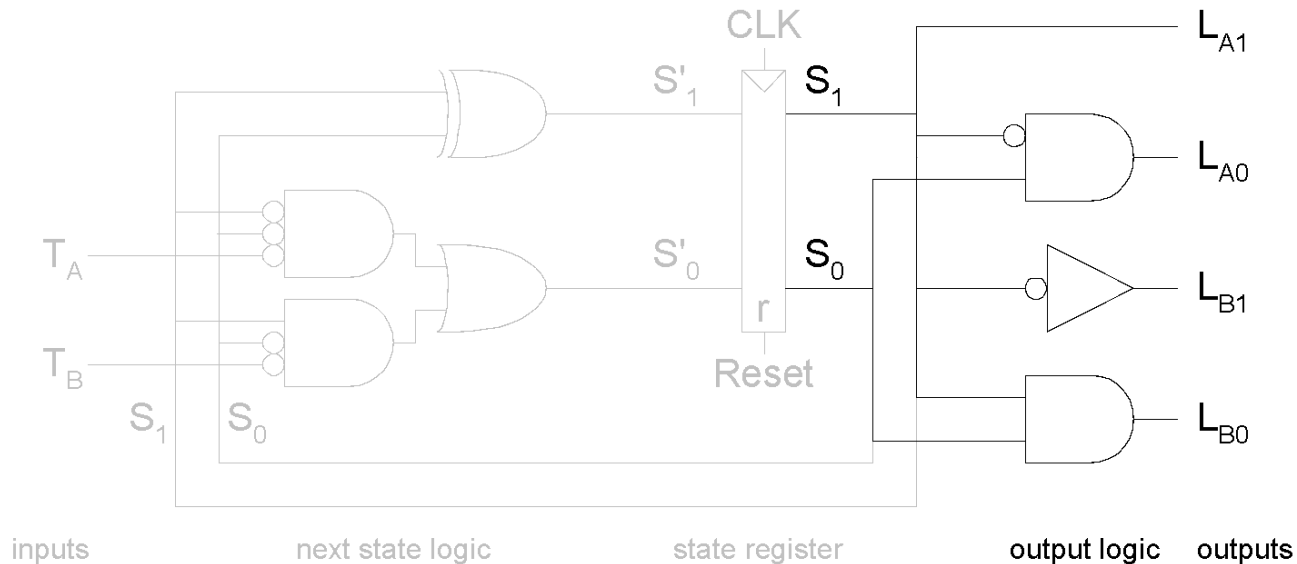

$$L_{A1} = S_1$$



$$L_{A0} = S_1 \cdot S_0$$

$$L_{B1} = S_1$$

$$L_{B0} = S_1 \cdot S_0$$

FSM Timing Diagram


45

  

FSM State Encoding

46

 - How do we encode the state bits?
 - **Three common state binary encodings** with **different tradeoffs**
 1. Fully Encoded
 2. 1-Hot Encoded
 3. Output Encoded
- Let's see an example **Swiss** Semaphore with 4 states
 - Green, Yellow, Red, Yellow+Red



FSM State Encoding Types

47

1. Binary Encoding (Full Encoding):

- Use the minimum number of bits used to encode all states
 - Use $\log_2(num_states)$ bits to represent the states
- *Example states:* 00, 01, 10, 11
- **Minimizes** # flip-flops, but not necessarily output logic or next state logic

2. One-Hot Encoding:

- Each bit encodes a different state
 - Uses num_states bits to represent the states
 - Exactly 1 bit is “hot” for a given state
- *Example states:* 0001, 0010, 0100, 1000
- **Simplest design process** – very automatable
- **Maximizes** # flip-flops, **minimizes** next state logic

FSM State Encoding Types

48

3. Output Encoding:

- Outputs are **directly accessible** in the state encoding
- For example, since we have **3 outputs** (light color), encode state with **3 bits**, where each bit represents a color
- *Example states:* 001, 010, 100, 110
 - Bit₀ encodes **green** light output,
 - Bit₁ encodes **yellow** light output
 - Bit₂ encodes **red** light output
- **Minimizes** output logic
- Only works for Moore Machines (output function of state)

Which encoding to use?

49

Encoding:


Depends on the designer criteria **to optimize or follow constraints.**

Recall: Types of FSM

50

- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 1. **Moore FSM**: **outputs depend only on current state**

Moore FSM

 


Recall: Types of FSM

51


- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 1. **Moore FSM: outputs depend only on current state**

Moore FSM

 

1. **Mealy FSM: outputs depend on current state *and* inputs**

Mealy FSM

 


FSM: Moore vs Mealy



52

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
 - The snail smiles whenever the last two digits** it has crawled over are 01.
- Design **Moore and Mealy FSMs** of the snail's brain.

Moore FSM

 


Mealy FSM

  


Example Moore vs Mealy

53


Moore FSM

 

Mealy FSM

 

Mealy FSM: arcs indicate input/output

 

FSM Design Procedure

57

1. Identify **inputs and outputs**
2. **Sketch state transition diagram**
3. **Write state transition table**
4. **Select state encodings**
5. **For Moore** machine:
 - a. Rewrite state transition table with state encodings
 - b. Write output table
5. **For a Mealy** machine:

Rewrite combined state transition and output table with state encodings
6. **Write Boolean equations for next state and output logic**
7. **Sketch the circuit schematic**

Homework

58

- **Read the FSM Moore to Mealy conversion** (and backwards) in Piazza>resources>lecture notes.
- **Finish Chapter 3** from HH book.
- **Try solving the suggested exercises (check piazza).**

Outline

59

Introduction

Definitions

Finite State Machines

Conclusion

Conclusions

60

- **We introduced fundamentals concepts** finite state machines
- **We detailed the design of** finite state machines.
- **A sequential circuit with combinational circuit allows to implement a finite state machine.**
- We conclude that **complex design can be implemented as a digital circuit following design guidelines and defining state transitions.**

Finite State Machines

Computer Architecture



CS3501 – 2025I

PROF.: JGONZALEZ@UTEC.EDU.PE

